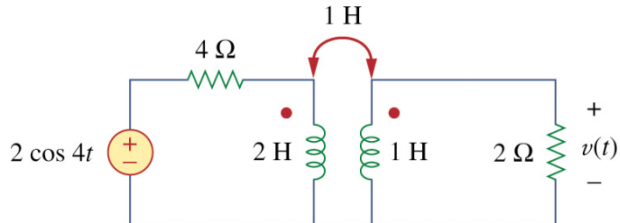


**This is the last homework assignment. Some of the content will require the lectures of December 4.**


**1:**

Find  $v(t)$  for the circuit below.




**2:**

Solve for  $v(t)$  in the circuit below

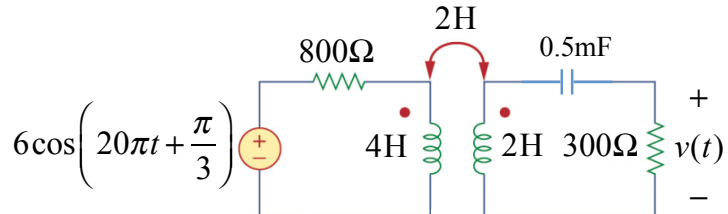


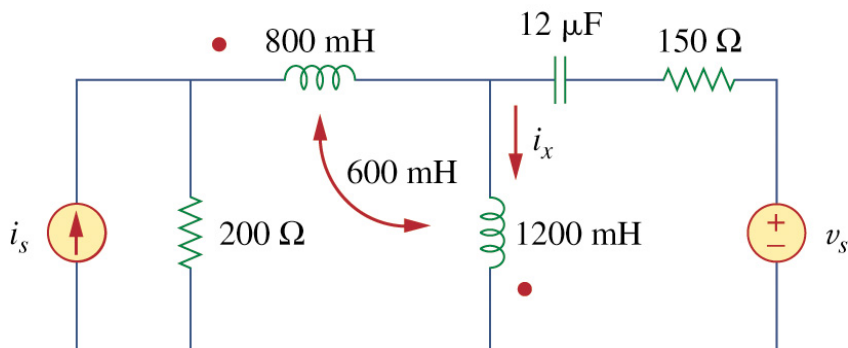**3:** Use mesh analysis to find  $i_x$  in the following circuit, when

$i_s = 4 \cos(600t)$ ,  $v_s = 110 \cos(600t + 30^\circ)$  Hint: Source transformation of the current source, after which the mesh current flows through both 800 mH and 1200 mH, inducing mutual inductance from each!



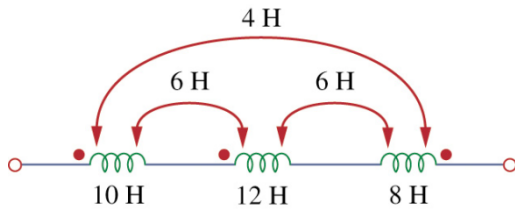
4: Determine the inductance of the three series-connected inductors shown below.



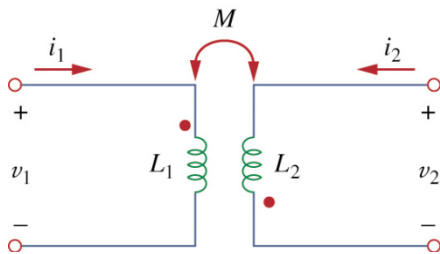
5:

The coils shown below have  $L_1 = 40\text{mH}$ ,  $L_2 = 5\text{mH}$ , and  $k = 0.6$ . (Pay attention to the defined direction of the currents!) Find  $i_1(t)$ ,  $v_2(t)$  given that

$$v_1(t) = 10 \cos \omega t, i_2(t) = 2 \sin \omega t, \omega = 2000 \text{ rad/sec}$$



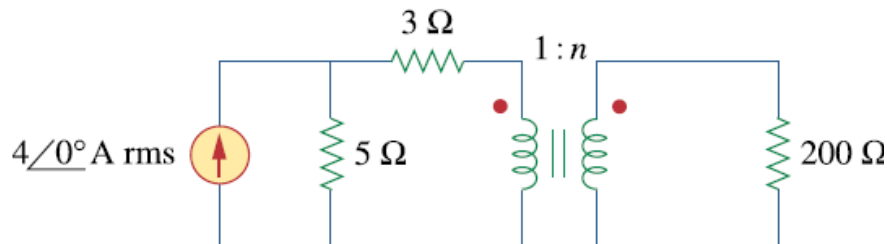6: Find  $n$  for the maximum power supplied to the  $200 \text{ ohm}$  load. Then determine the power to the  $200 \text{ ohm}$  load if  $n=10$ .



7:

Obtain the transfer function  $\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}$  of the following circuit. **Note** that there is a "typo" in the circuit figure, and the voltage source should be labeled  $\mathbf{V}_i$ .

